

# Hardware Design using Verilog

Sayandeep Saha

Assistant Professor  
Dept. of CSE, IIT Bombay

# Overview

Glossary: what terms will we cover in this lecture..

**FPGA**

**LUT and CLB**

**Comparison between FPGA, ASIC  
and Microcontroller**

**HDLs**

**FPGA design flow**

**Introduction to Verilog**

**Verilog Data Types**

**Module Hierarchy**

**Assignments**

**Parameters**


**Testbench**

**Simulation**

# Introduction to FPGA

 
# What is Electronic Design?

- Process of developing a circuit by using **known** electronic components in order to meet the given **specifications**.
- Specifications: detailed description of desired behavior of the circuit
- Known devices: devices whose behavior can be modeled by known equations or algorithms, with known values of parameters



 
# Electronic Design

- Process of converting a behavioral description of a circuit to a structural description.
- After the conversion, comes the **physical design** which involves choosing component sizes, their physical arrangement, defining the connections.
- Physical design is already done in **FPGA** based design.



 
# Are standard chips the best choice?

- Functions provided by these chips are fixed and inefficient for building large circuits.
- Need for a chip suitable for large logic circuitry where structure is not fixed.
- **PLD** (Programmable Logic Device): general-purpose chip with a pool of logic gates and programmable switches.




# PLD example: FPGA

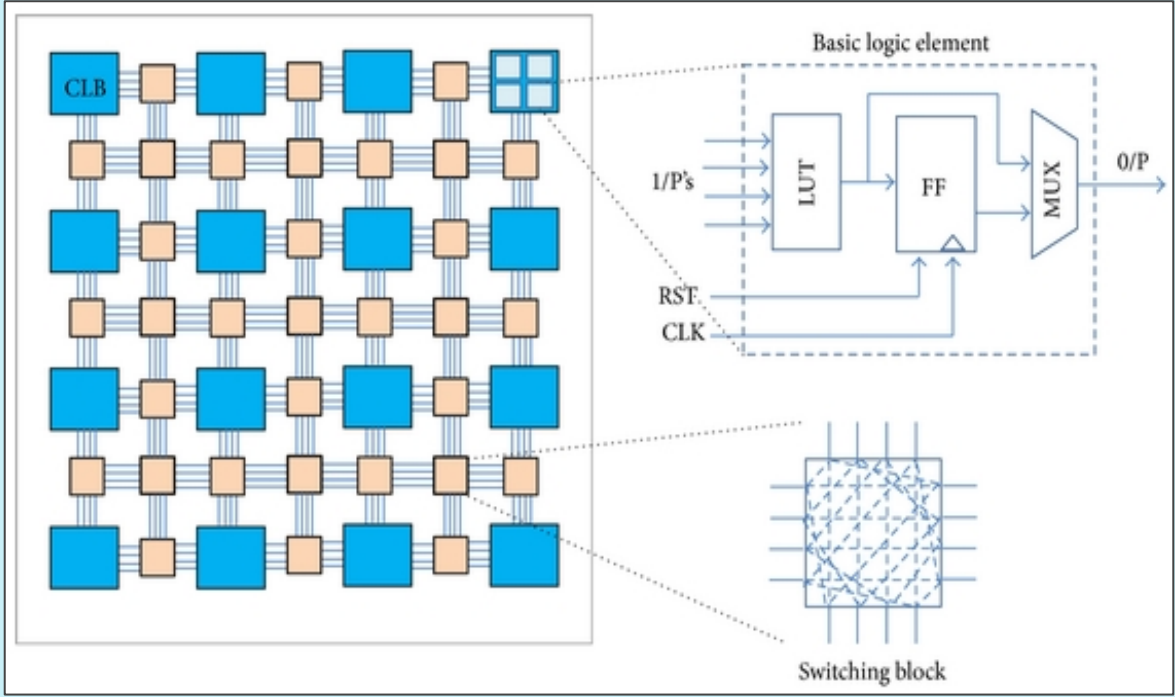
 
# PLD example: FPGA


- FPGA: an array of pre-placed, prefabricated configurable logic blocks/elements (CLBs)
- These blocks are also connected by a prefabricated signal routing conductor path segments
  - Appropriate paths are stitched together by configuring switches
  - Switches: pass-transistors



# Comparison between FPGA, ASIC and Microcontroller & Applications

# FPGA vs ASIC

FPGA

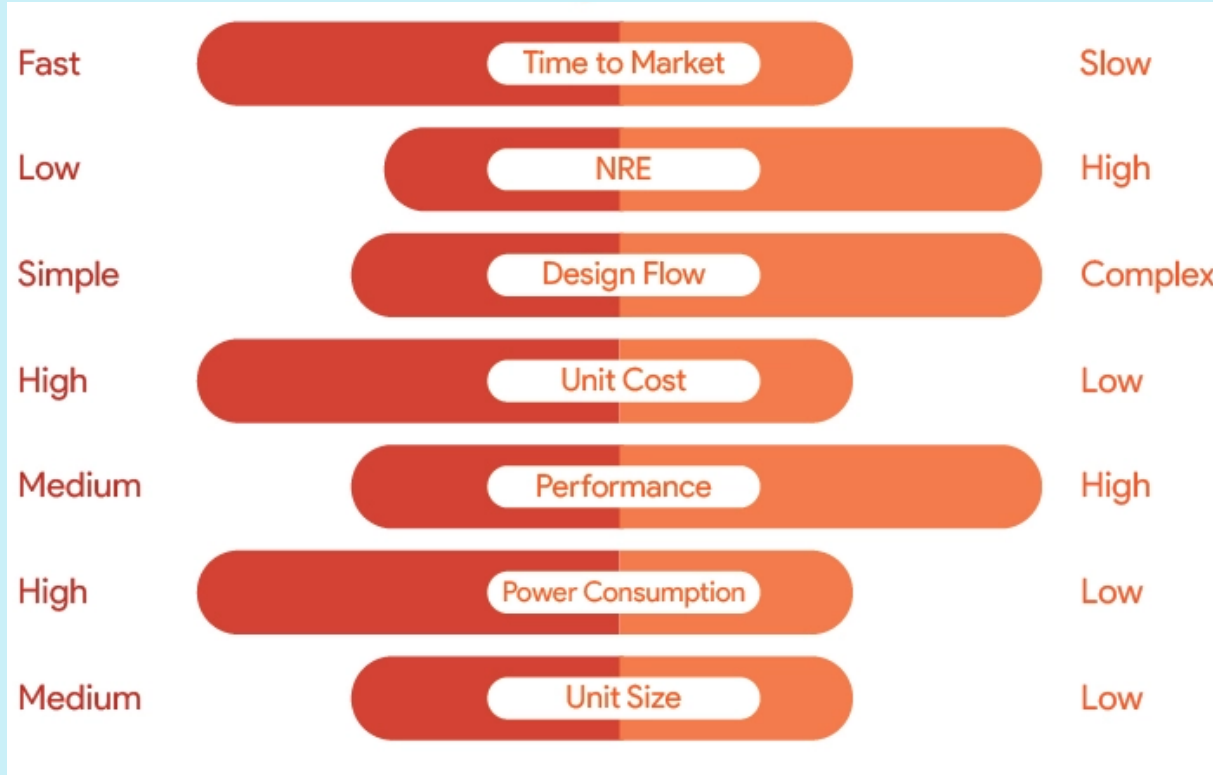

ASIC

# FPGA vs Microcontroller

FPGA	Microcontroller
<ul style="list-style-type: none"><li>● All parts of circuit operate independently</li><li>● Max. clock speed depends on design</li><li>● Many IOs can be accessed simultaneously</li><li>● Power usage depends on design but typically more than microcontroller</li><li>● Relatively costly</li></ul>	<ul style="list-style-type: none"><li>● Executes one instruction at a time</li><li>● Fixed max. clock speed</li><li>● Limited IOs (typically 8) can be accessed at a time</li><li>● Often very power efficient with advanced sleep modes</li><li>● Relatively cheap</li></ul>

# Applications of FPGA


- Prototyping
  - Ensemble of gate arrays used to emulate a circuit before manufacturing
  - Faster and more accurate simulation
- Less cost production
  - Very less time to market
- Reconfigurable Computing
  - Same hardware used to configure on the fly!
- Special Purpose Computing Platform
  - Dedicated to solve one problem
  - Can be attached to general purpose computers

# HDLs and FPGA Design Flow

# Hardware Description Languages (HDLs)

- A computer language used to describe the structure and behavior of electronic circuits (usually digital circuits).
  - Need for HDLs
    - Circuits were designed on PCBs, test and design of large circuits not easy
    - HDL: easy to describe hardware circuits in terms of software algorithm with a particular syntax
    - CAD tools now generate the complex hardware circuit from the HDL algorithm
- **Verilog**
- VHDL (Very High Speed Integrated Circuit Hardware Description Lang.)

# FPGA Design Flow

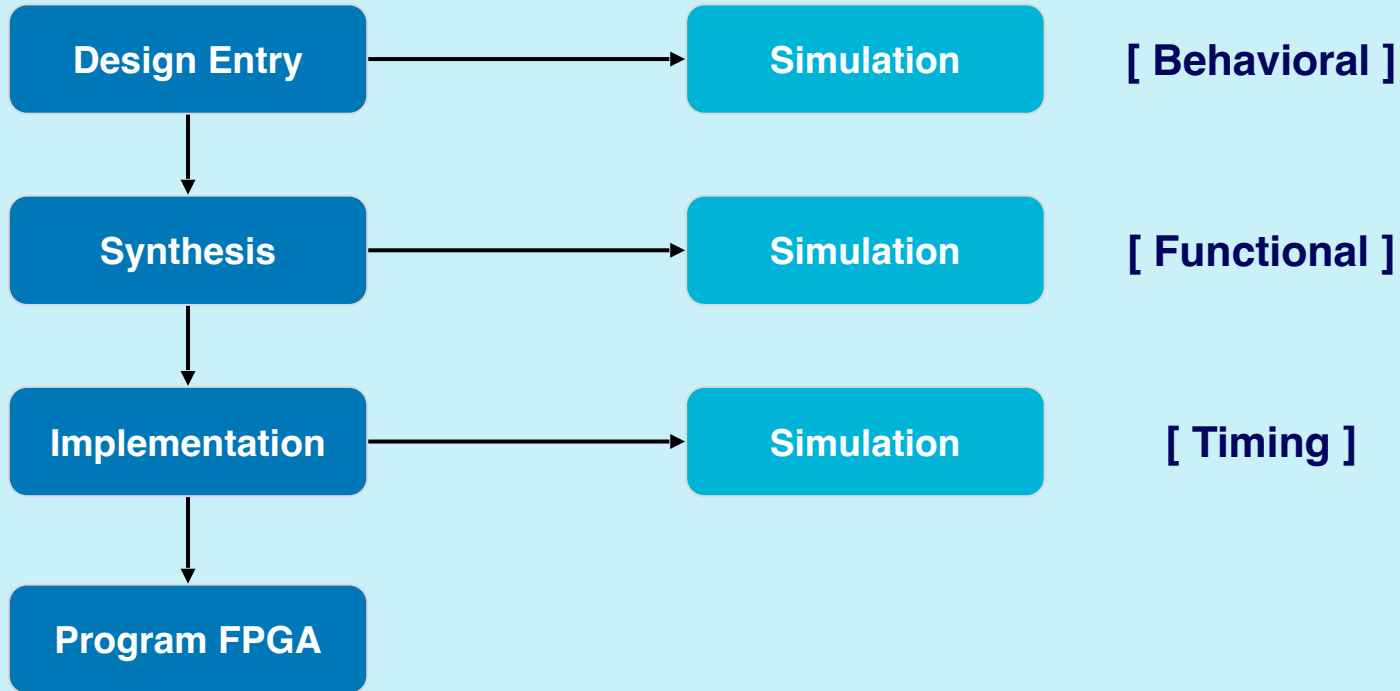

**Any Questions?**

# Introduction to Verilog

# Verilog language

- Originally a modeling language for a very efficient event-driven digital logic simulator.
- Later pushed into use as a specification language for logic synthesis.
- One of the two most commonly-used languages in digital hardware design (other is VHDL).
- Virtually every chip (FPGA, ASIC, etc.) is designed in part using one of these two languages.

# Logic Simulation and Synthesis

- Logic Simulation
  - Runs your circuit in computer before you map it to silicon.
  - Essential for ensuring correctness, testing, etc.
- Logic Synthesis
  - Converts your logic described in high-level to a gate-level description => equivalent to a compiler.
  - Register-transfer level (RTL) to gates conversion
  - Such compilation also involves logic minimization

# Concurrency


- Verilog or any HDL has the power to model concurrency which is natural to a piece of hardware.
- There may be two hardware circuits that are independent of each other.
- Verilog provides the following constructs for concurrency:
  - always
  - assign
  - module instantiation
  - non-blocking assignments inside a sequential block

# Multiplexer built with primitives (structural modelling)

Verilog programs built from modules

Each module has an interface

 Module may contain structure: instances of primitives and other modules



```
module mux (f, a, b, sel);
input a, b, sel;
output f;

wire f1, f2;

and g1 (f1, a, nsel),
      g2 (f2, b, sel);
or g3 (f, f1, f2);
not g4 (nsel, sel);

endmodule
```

# Verilog logic values


- Predefined logic value system or value set to:
  - '0', '1', 'x' or 'z'
- 'x' means uninitialized or unknown logic value
- 'z' means high impedance value

# Verilog data types

- Nets: wire
  - Analogous to a wire in an ASIC
  - Cannot store or hold a value
  - To model connectivity, any value driven by a device must be driven continuously onto that wire, in parallel with the other driving values.
- Integer: used for the index variables of say for loops. No hardware implication.
 
# Multiplexer built with primitives (structural modelling)

Identifiers not explicitly defined default to wires




```
module mux (f, a, b, sel);  
input a, b, sel;  
output f;  
  
wire f1, f2;  
  
and g1 (f1, a, nsel),  
      g2 (f2, b, sel);  
or g3 (f, f1, f2);  
not g4 (n.sel, sel);  
  
endmodule
```
 
# Multiplexer built with always (behavioral modelling)

Modules may contain one or more *always* blocks

Sensitivity list contains the signals whose change triggers the execution of the block




```
module mux (f, a, b, sel);  
input a, b, sel;  
output f;  
  
reg f;  
  
always @(a or b or sel) begin  
    if (sel) f = b;  
    else f = a;  
  
end  
  
endmodule
```
 
# Multiplexer built with always (behavioral modelling)

A *reg* behaves like memory:  
holds its value until imperatively  
assigned otherwise

Body of an *always* block contains  
traditional imperative code



```
module mux (f, a, b, sel);  
input a, b, sel;  
output f;
```

```
reg f;
```

```
always @(a or b or sel) begin  
    if (sel) f = b;  
    else f = a;
```

```
end
```

```
endmodule
```

# The *reg* data type

- Register data type: similar to a variable in programming language
- Default initial value: 'x'
- ```
module reg_ex1;  
  reg q; wire d;  
  always @(posedge clk) q = d;
```
- A reg is not always equivalent to a hardware register, flip-flop or latch
- ```
module reg_ex2; // purely combinational  
  reg c;  
  always @(a or b) c = alb;
```

# The *reg* data type

- Programming languages provide variables that can contain arbitrary values of a particular type.
- They are implemented as simple memory locations.
- Assigning a value to such variables is like storing the value at the memory location.
- Verilog *reg* operates in the same way.
- Previous assignments have no effect on the final result.

# Example of *reg*

```
module assignments;  
reg r;
```

```
initial r <= #20 3;  
initial begin  
    r = 5; r <= #35 2;
```


```
end  
initial begin  
    r <= #100 1;  
    #15 r = 4;  
    #220;  
    r = 0;
```

```
end  
endmodule
```

- The variable *r* is shared by all the concurrent blocks.
- *r* takes the value that was last assigned.
- This is *like* a hardware register which also stores the value that was last loaded into it.
- But a *reg* is **not necessarily** a hardware register.
 
# Multiplexer with assign (dataflow modelling)

LHS is always set to the value on the RHS  
Any change on the RHS causes re-evaluation



```
module mux (f, a, b, sel);  
input a, b, sel;  
output f;  
  
assign f = sel ? b : a;  
  
endmodule
```

Any Questions?

# Module Hierarchy and Instantiation

- Module interface provides the means to interconnect two Verilog modules.
- Note that a **reg** cannot be an **input** or **inout** port.
- A module may instantiate other modules.
- Instances of `module mymod (y, a, b);` can be of two ways:
  - Connect-by-position: `mymod mm1 (y1, a1, b1);`
  - Connect-by-name: `mymod mm2 (.a(a2), .b(b2), .y(y2));`

# Sequential blocks and Procedures

- Sequential block is a group of statements between a **begin** and an **end**.
- A sequential block, in an **always** statement executes repeatedly.
- Inside an **initial** statement, it executes only once.
- A procedure is an **always** or **initial** statement or a function.
- Procedural statements within a sequential block executes concurrently with other procedures.

# Assignments

- Let's see the various module assignments
- `module xyz ();`  
`// continuous assignments`  
`always // beginning of a procedure`  
`begin // beginning of a sequential block`  
`// ..... procedural assignments`  
`end`  
`endmodule`
- A continuous assignment assigns a value to a wire like a real gate driving a wire.

# Assignments example

```
module holiday_1 (sat,sun,weekend);  
input sat, sun;  
output weekend;
```

```
// continuous assignment  
assign weekend = sat | sun;
```

```
endmodule
```

```
module holiday_2 (sat,sun,weekend);  
input sat, sun;  
output weekend;
```

```
reg weekend;
```

```
always @(sat or sun)  
    // procedural assignment  
    weekend = sat | sun;
```

```
endmodule
```

# Blocking and Non-blocking assignments

- Blocking procedural assignments must be executed **before** the procedural flow can pass to the subsequent statement.
- A non-blocking procedural assignment is **scheduled** to occur **without** blocking the procedural flow to subsequent statements.

`a = 1; b = a; c = b;`

Blocking assignment:

`a = b = c = 1`

`a <= 1; b <= a; c <= b;`


Non-blocking assignment:

`a = 1`  
`b = old value of a`  
`c = old value of b`


# Non-blocking looks like latches!

- RHS of non-blocking taken from latches
- RHS of blocking taken from wires

$a = 1; b = a; c = b;$

 

$a \leq 1; b \leq a; c \leq b;$

 

# Examples

```
// blocking assignment
always @(a1 or b1 or c1 or m1) begin
    m1 = #3 (a1 & b1);
    y1 = #1 (m1 | c1);
end
```

Statement executed at time  $t$   
causing  $m1$  to be assigned at  $t+3$

Statement executed at time  $t+3$  causing  
 $y1$  to be assigned at time  $t+4$

```
// non-blocking assignment
always @(a2 or b2 or c2 or m2) begin
    m2 <= #3 (a2 & b2);
    y2 <= #1 (m2 | c2);
end
```

Statement executed at time  $t$   
causing  $m2$  to be assigned at  $t+3$

Statement executed at time  $t$  causing  
 $y2$  to be assigned at time  $t+1$ .  
Uses old values.

# Numbers

- Format of integer constants:  
width' radix value;
- Verilog keeps track of the sign if it is assigned to an integer or assigned to a parameter.
- Once Verilog loses the sign the designer has to be careful.

# Parameterized design

```
module vector_and (z, a, b);  
parameter cardinality = 1;  
input [cardinality-1:0] a, b;  
output [cardinality-1:0] z;  
    wire [cardinality-1:0] z = a & b;  
endmodule
```


```
module four_and_gates (outbus, inbus_a, inbus_b);  
input [3:0] inbus_a, inbus_b; output [3:0] outbus;  
  
vector_and #(4) my_and(outbus, inbus_a, inbus_b);  
endmodule
```

Any Questions?

# Modelling Sequential Circuits

- `always @(posedge clk) begin <procedural_statements> end`
- “posedge clk” means that the value in the flip-flops change at the positive edge of the clk
- “negedge clk” can also be used
- `@(sensitivity_list)` triggers the always block when one of the signals in the list changes

# Car Speed Controller

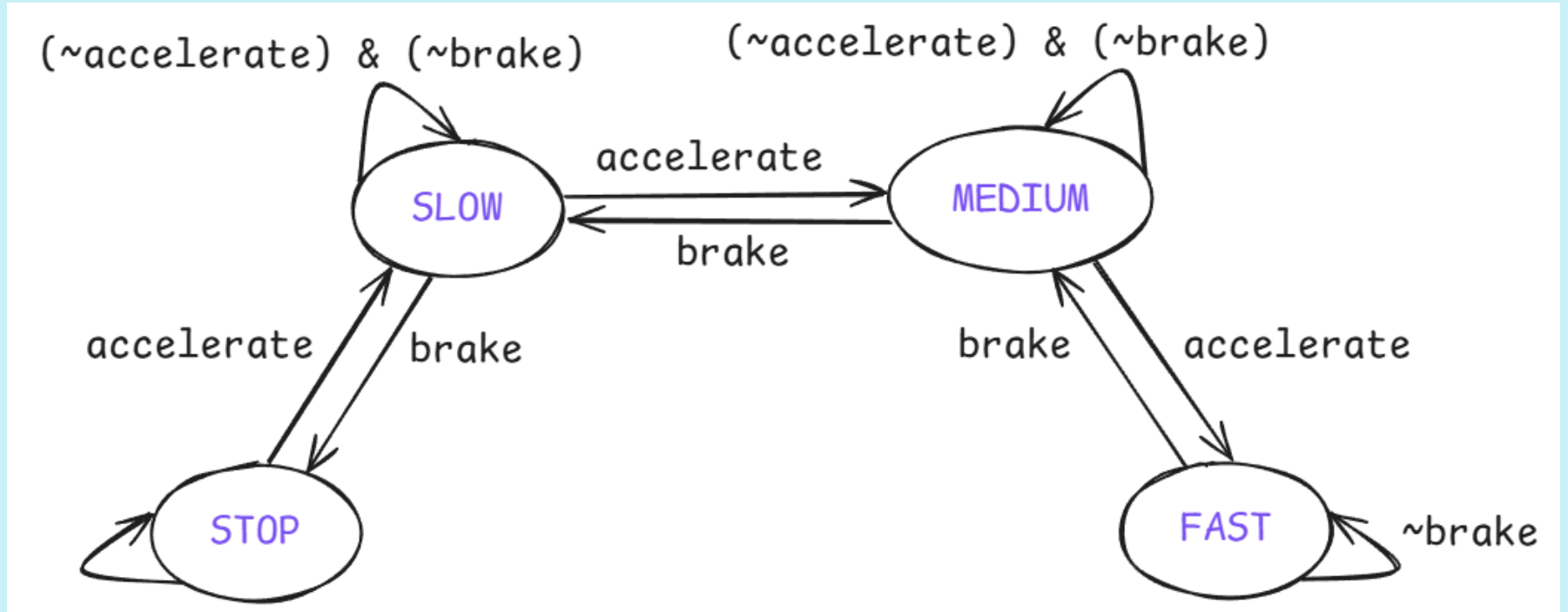

# Car Speed Controller Code (I)

```
module fsm_car_speed1 (clk,keys,accelerate,brake,speed);  
input clk, keys, accelerate, brake;  
output [1:0] speed;  
  
reg [1:0] speed;  
  
// states of speed  
parameter          stop = 2'b00,  
                    slow = 2'b01,  
                    mdium = 2'b10,  
                    fast = 2'b11;
```

# Car Speed Controller Code (II)

```
always @(posedge clk or
        negedge keys)
begin
if (!keys)
    speed = stop;
else if (accelerate)
    case (speed)
        stop: speed =
slow;
        slow: speed =
mdium;
        mdium: speed =
fast;
        fast: speed =
fast;
    endcase
else if (brake)
    case (speed)
        stop: speed =
stop;
        slow: speed =
stop;
        mdium: speed =
slow;
        fast: speed =
mdium;
    endcase
else
    speed = stop;
end
endmodule
```

# Car Speed Controller: a better way!

- We keep a separate control part where the next state is computed.
- The other part generates the output from the next state.
- We follow this architecture in the implementation of any finite state machines, like ALU, CPU, etc.

# Car Speed Controller [better] Code

```
module fsm_car_speed2 (clk,keys,accelerate,brake,speed);
input clk, keys, accelerate, brake;
output [1:0] speed;

reg [1:0] speed; reg [1:0] newspeed;

// states of speed
parameter          stop = 2'b00,
                   slow  = 2'b01,
                   mdium = 2'b10,
                   fast  = 2'b11;
```

```

// datapath
always @(keys or accelerate or
        brake or speed)
begin
case (speed)
        stop:
        if (accelerate)
            newspeed = slow;
        else
            newspeed = stop;
        slow:
        if (brake)
            newspeed = stop;
        else if (accelerate)
            newspeed = mdium;
        else
            newspeed = slow;
mdium:
        if (brake)
            newspeed = slow;
        else if (accelerate)
            newspeed = fast;
        else
            newspeed = mdium;
endcase
end

```

```

        fast:
        if (brake)
            newspeed = mdium;
        else
            newspeed = fast;
        default:
            newspeed = stop;
    endcase
end

// controller
always @(posedge clk or negedge keys)
begin
    if (!keys)
        speed = stop;
    else
        speed = newspeed;
end

endmodule

```

# Conclusion


- Write codes which can be translated into hardware!
- Following cannot be translated into hardware (non-synthesizable)
  - **initial** blocks
    - Used to set up initial state or describe finite testbench stimuli
    - Don't have obvious hardware component
  - **Delays**
    - Maybe in the Verilog source, but are simply ignored
- Finally, remember that you are a better designer than the tool.

Any Questions?



# Behavioral Simulation
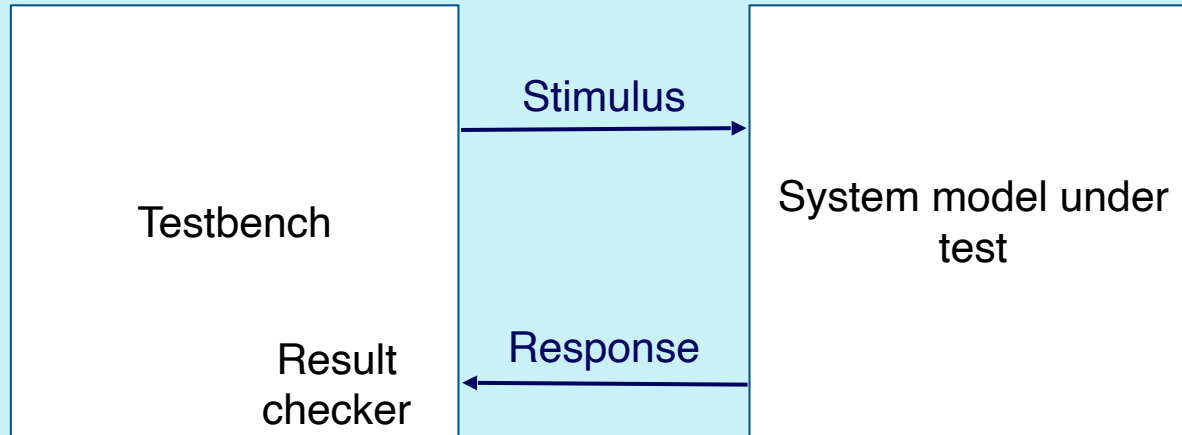
# How do we test the behavior of a design?

- Testbench generates stimulus and checks response
- Coupled to model of the system under test
- Testbench and system under test are run simultaneously



# Looking back at the multiplexer design

  

```
// dataflow modelling  
module mux2 (in0,in1,sel,out);  
input in0, in1, sel;  
output out;
```

```
assign out = (~sel & in0)
```

```
(sel & in1);
```


```
// alternative  
// assign out = sel ? in1 : in0;
```

```
endmodule
```
 
# Testbench for the multiplexer

```
`timescale 1ns/1ps
module testmux;
reg a, b, s;
wire f;
reg expected;

mux2 dut (.sel(s), .in0(a), .in1(b), .out(f));
initial begin
$monitor ("sel=%b in0=%b in1=%b out=%b,expected out=%b time=%d",s,a,b,f,expected,$time);
    s = 0; a = 0; b = 1; expected = 0;
    #10 a = 1; b = 0; expected = 1;
    #10 s = 1; a = 0; b = 1; expected = 1;
    #10 a = 1; b = 0; expected = 0; #10;
end
initial begin
    $dumpfile ("dump.vcd");
    $dumpvars (1, testmux);
end
endmodule
```



Any Questions?

# Some more design examples


# Recap...

- Break the design into data path and control path.
- Datapath is mostly combinational.
- Controller is the sequential logic which sends control signal to the data path.
- Always start by drawing the data path.
- Then identify the control signals.
- Make a module for data path components, this may contain many submodules
- Make a separate module for the controller (optional but recommended).
- Instantiate and connect everything in a top module.
- Top module will contain multiple combinational and sequential blocks.

# Ripple Carry Adder
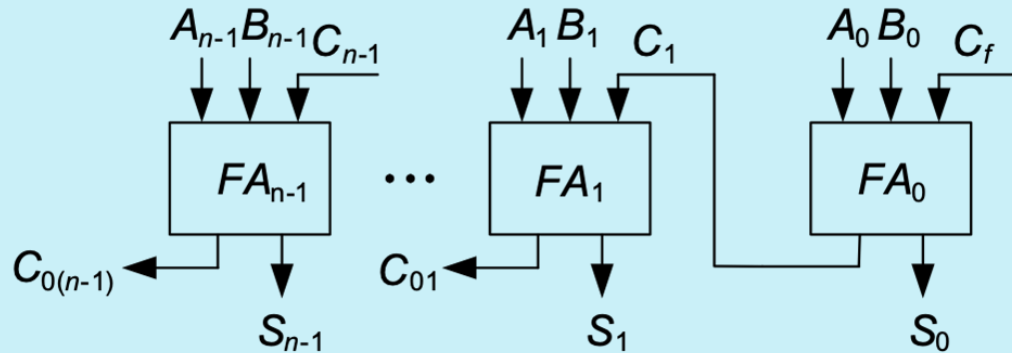
# Ripple Carry Adder

- Consists of N cascaded stages of full adder.



$C_f$  : forced carry

$C_{0(n-1)}$  : overflow carry

$$S_i = A_i \oplus B_i \oplus C_i$$

$$C_{0i} = A_i B_i + B_i C_{0(i-1)} + C_{0(i-1)} A_i$$

# Code for 4-bit Ripple Carry Adder

```
module full_adder (a, b, cin, s, cout);  
input a, b, cin;  
output s, cout;
```

```
assign s = a ^ b ^ cin;  
assign cout = (a & b) | (cin & (a ^ b));
```


```
endmodule
```

```
module adder_4bit (a, b, cin, s, cout);  
input [3:0] a, b; input cin;  
output [3:0] s; output cout;
```

```
wire c1, c2, c3;
```

```
full_adder fa1 (.a(a[0]), .b(b[0]), .cin(cin), .s(s[0]), .cout(c1));  
full_adder fa2 (.a(a[1]), .b(b[1]), .cin(c1), .s(s[1]), .cout(c2));  
full_adder fa3 (.a(a[2]), .b(b[2]), .cin(c2), .s(s[2]), .cout(c3));  
full_adder fa4 (.a(a[3]), .b(b[3]), .cin(c3), .s(s[3]), .cout(cout));
```

```
endmodule
```

 

# Code for N-bit Ripple Carry Adder

```
// n-bit ripple carry adder
module nbit_rca #(parameter N = 32) (a, b, cin, s, cout);
input [N-1:0] a, b; input cin;
output [N-1:0] s; output cout;

wire [N:0] cr;
assign cr[0] = cin;

generate
    genvar i;
    for (i = 0; i < N; i = i + 1) begin : full_adder_instance
        full_adder fa (.a(a[i]), .b(b[i]), .cin(cr[i]), .s(s[i]), .cout(cr[i+1]));
    end
endgenerate

assign cout = cr[N];

endmodule
```

# Testbench for N-bit Ripple Carry Adder

```
`timescale 1ns/1ps
module tb_nbit_rca;
parameter N = 32;

reg clk; reg rst;
reg [N-1:0] A; reg [N-1:0] B; reg Cin;
wire [N-1:0] S; wire Cout;
```

initial begin

```
$display ("time\t, clk\t, rst\t, A\t, B\t, Cin\t, S\t, Cout");
$monitor ("%g\t %b\t %b\t %d\t %d\t %b\t %d\t %b\t", $time, clk, rst, A, B, Cin, S, Cout);
```


```
clk = 1; rst = 0;
#10 rst = 1; #10 rst = 0;
#10 A = 4294967295; #10 B = 4294967295; Cin = 0;
#10 A = 4294967294; #10 B = 4294967294;
#20; #5 $finish;
```

end

always begin

```
#5 clk = ~clk;
```

end

 

```
nbit_rca #(N) dut (.a(A), .b(B), .cin(Cin), .s(S), .cout(Cout));
```

initial begin

```
$dumpfile ("nbit_rca.vcd");
$dumppvars (1, tb_nbit_rca);
```

end

endmodule

# Counter

# Code for 4-bit Up Down Counter

```

module up_down_counter (clk, rst, up_down, out);
input clk, rst, up_down;
output [3:0] out;

```

```

reg [3:0] out;

```

```

always @(posedge clk) begin
    if (rst)

```

```

        out <= 4'b0;
    else if (up_down)

```

```

        out <= out + 1;
    else

```

```

        out <= out - 1;
    end

```

```


end

```

```

endmodule

```

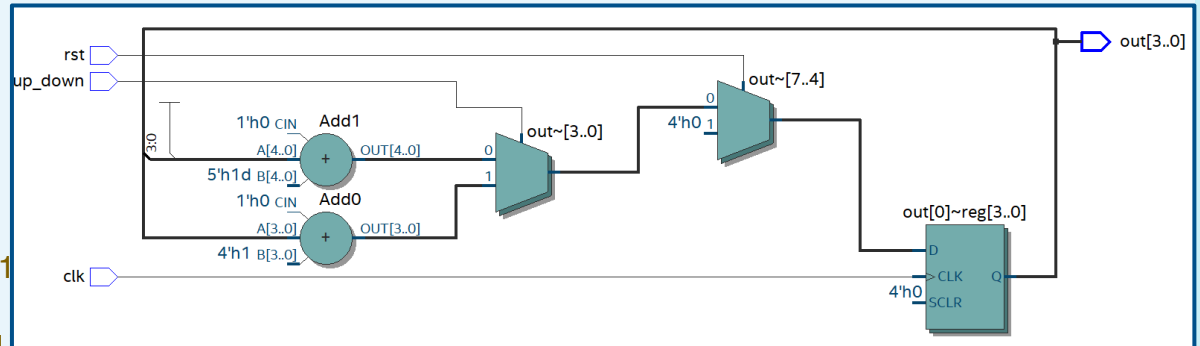


# Testbench for 4-bit Up Down Counter

```
`timescale 1ns/1ps
module tb_up_down_counter;
reg clk, rst, up_down;
wire [3:0] count;

initial begin
    $display ("time\t, clk\t, rst\t, up_down\t, count");
    $monitor ("%g\t %b\t %b\t %b\t %d", $time, clk, rst, up_down, count);

    clk = 1; rst = 0;
    #10 rst = 1; up_down = 1; #10 rst = 0;
    #70 up_down = 0; #50 up_down = 1; #60 up_down = 0;
    #20; #5 $finish;
end
always begin
    #5 clk = ~clk;
end

 up_down_counter dut (.clk(clk), .rst(rst), .up_down(up_down), .out(count));
initial begin
    $dumpfile ("up_down_counter.vcd"); $dumpvars (1, tb_up_down_counter);
end
endmodule
```



# Karatsuba Multiplier

# Karatsuba algorithm

- Basic principle: divide-and-conquer
- Computes product of two numbers  $\mathbf{x}$  and  $\mathbf{y}$  using three multiplications of smaller numbers, each having half the digits as  $\mathbf{x}$  or  $\mathbf{y}$ , and some additions and logical shifts.

# Karatsuba algorithm

- Let  $\mathbf{x}$  and  $\mathbf{y}$  be  $n$ -digit strings in base  $\mathbf{B}$ . For any positive integer  $\mathbf{m}$  less than  $\mathbf{n}$ , we can write,

$$\mathbf{x} = \mathbf{x}_1\mathbf{B}^m + \mathbf{x}_0 \text{ and } \mathbf{y} = \mathbf{y}_1\mathbf{B}^m + \mathbf{y}_0$$

where  $\mathbf{x}_0$  and  $\mathbf{y}_0$  are less than  $\mathbf{B}^m$ .

- The product is then,

$$\begin{aligned}\mathbf{xy} &= (\mathbf{x}_1\mathbf{B}^m + \mathbf{x}_0)(\mathbf{y}_1\mathbf{B}^m + \mathbf{y}_0) \\ &= \mathbf{x}_1\mathbf{y}_1\mathbf{B}^{2m} + (\mathbf{x}_1\mathbf{y}_0 + \mathbf{x}_0\mathbf{y}_1)\mathbf{B}^m + \mathbf{x}_0\mathbf{y}_0 \\ &= \mathbf{z}_2\mathbf{B}^{2m} + \mathbf{z}_1\mathbf{B}^m + \mathbf{z}_0\end{aligned}$$

# Karatsuba algorithm

- The product is then,

$$\mathbf{xy} = \mathbf{z_2B^{2m} + z_1B^m + z_0}$$

where  $\mathbf{z_2 = x_1y_1}$  ,  $\mathbf{z_1 = x_1y_0 + x_0y_1}$  ,  $\mathbf{z_0 = x_0y_0}$

- Karatsuba's contribution:


with  $\mathbf{z_2}$  and  $\mathbf{z_0}$  as before and  $\mathbf{z_3 = (x_1 + x_0)(y_1 + y_0)}$ ,

$$\mathbf{z_1 = x_1y_0 + x_0y_1}$$

$$\mathbf{= (x_1 + x_0)(y_1 + y_0) - x_1y_1 - x_0y_0}$$

$$\mathbf{= z_3 - z_2 - z_0}$$

# Datapath of Karatsuba multiplier

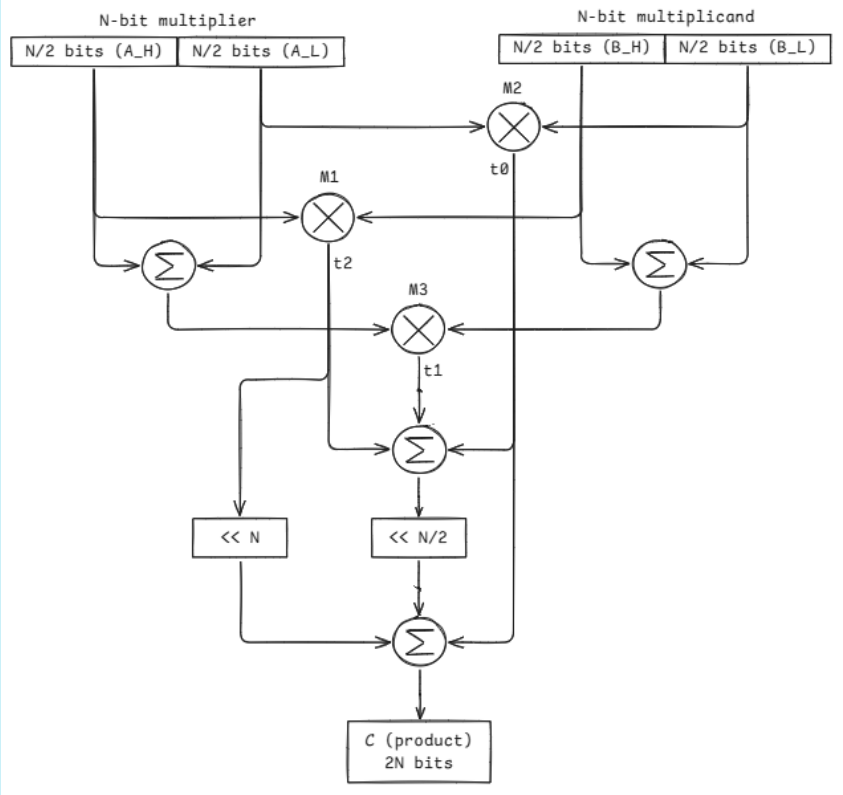

# Composite Function

# Problem statement

- Goal: Let's say we have a function  $y = f(x) = (A \& x) \wedge B$  where **A** and **B** are constants
- You have to implement the below functionality


```
while (counter <= 31):
```

```
    x = f(x);
```

```
    counter++;
```


# How to design the datapath?

- Let's draw the design in steps

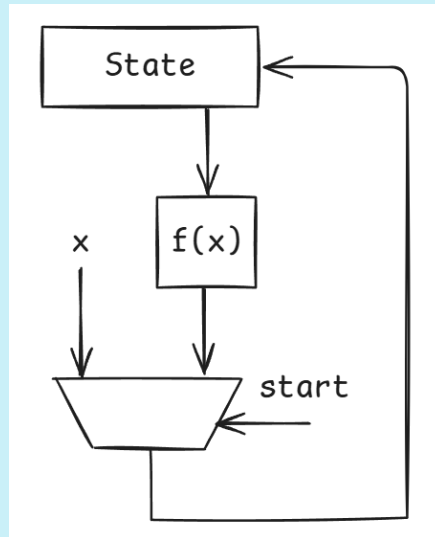

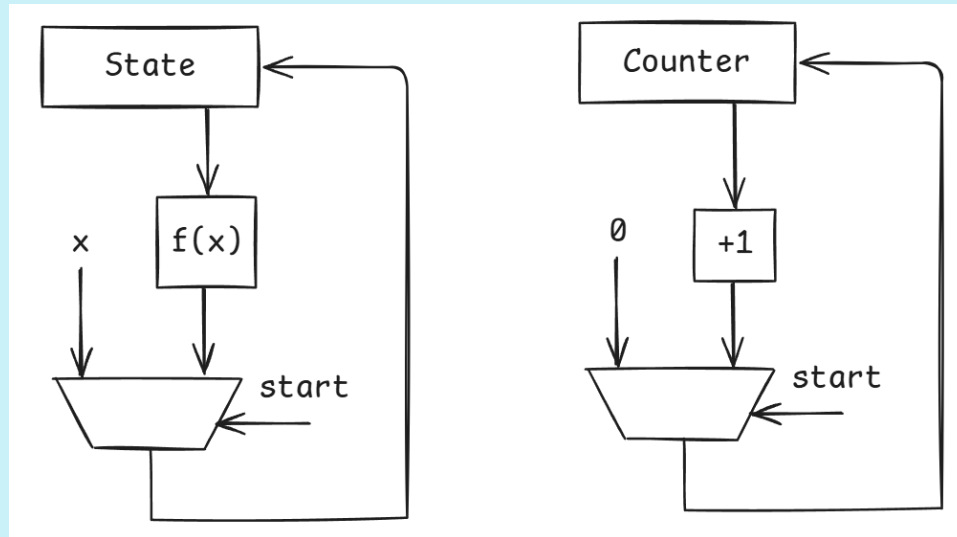
# How to design the datapath?

- We also need a counter
- The counter counts and the state updates for each clock while start = 1




# How to design the datapath?

- Now let's bring in the controller

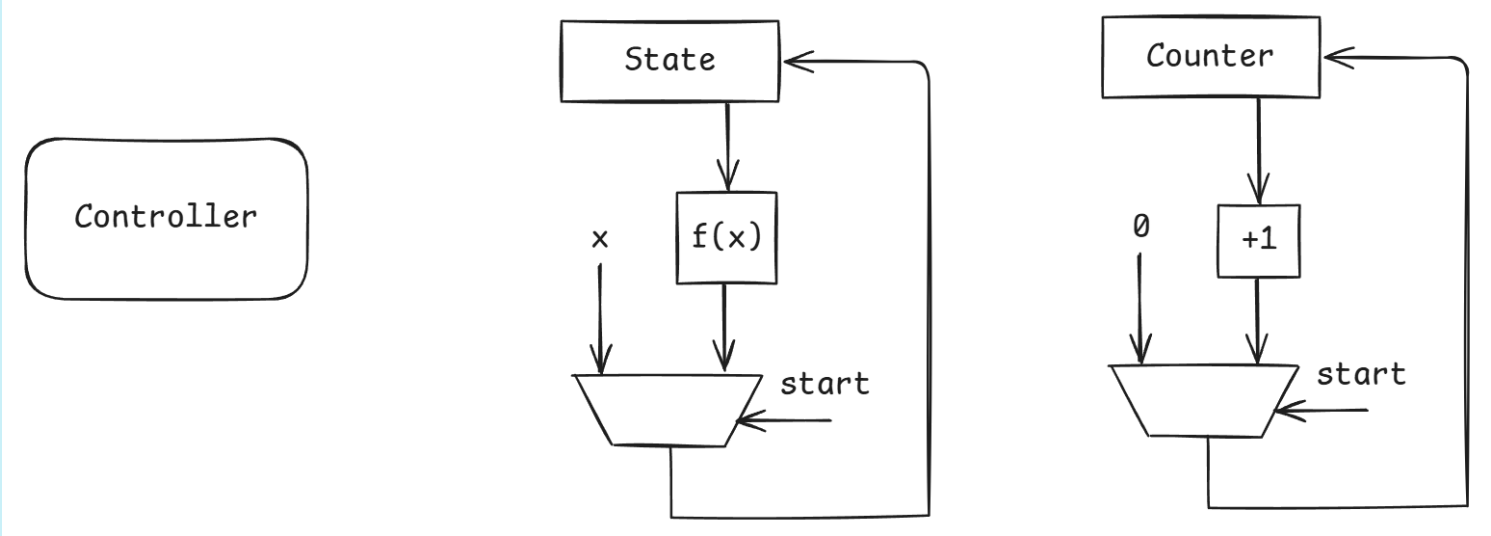

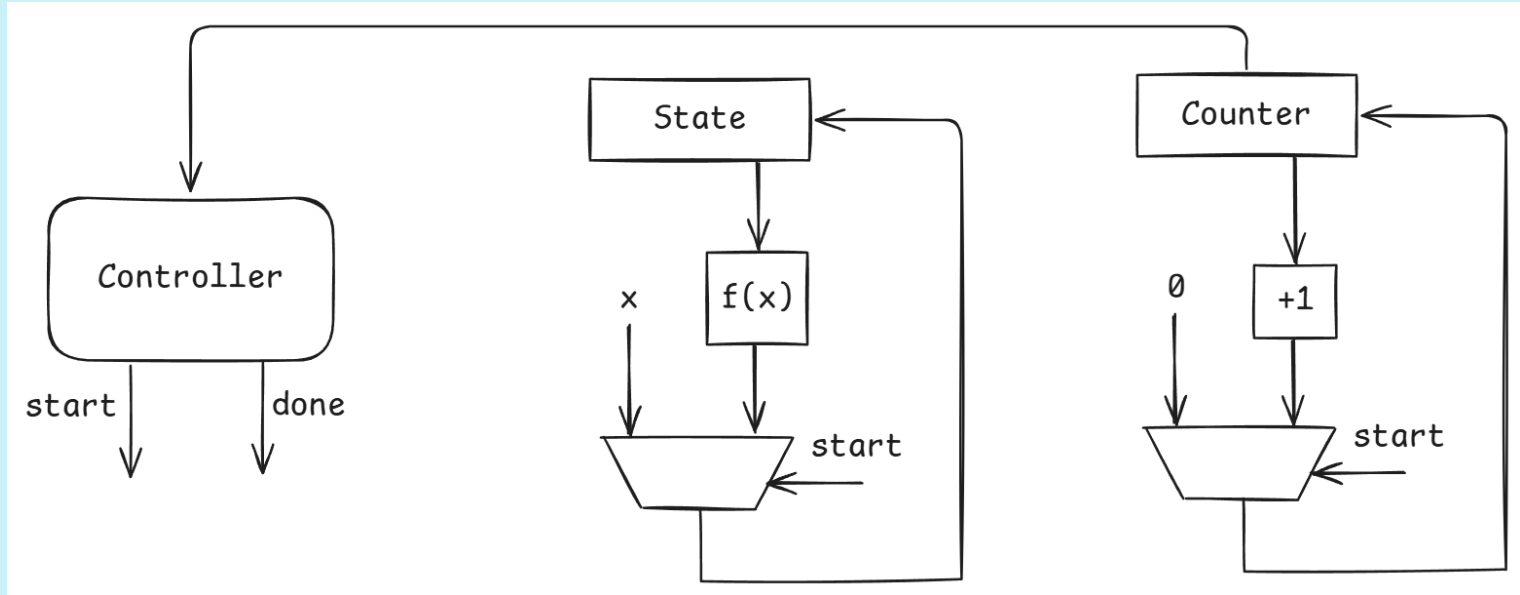
# How to design the datapath?

- The controller stops the circuit while counter == 31



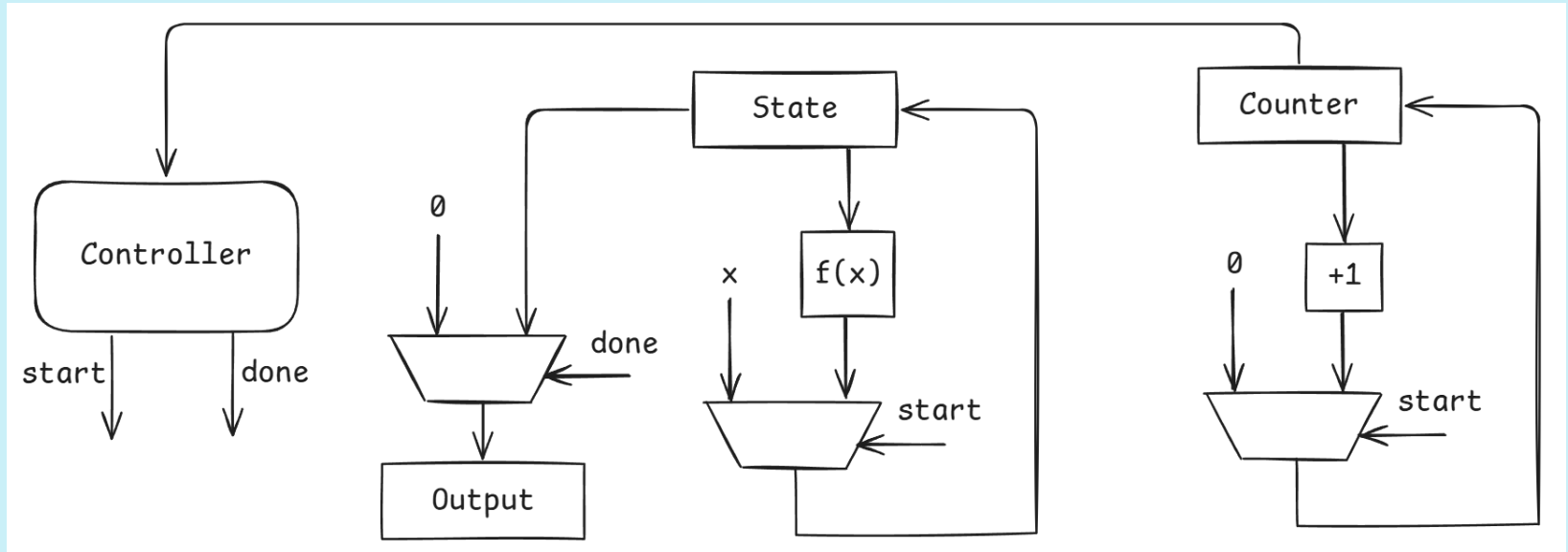
# How to design the datapath?

- The controller stops the circuit while counter == 31
- It also generates output at that point, controlled by “done” signal



# How to design the datapath?

- Some more essential input signals

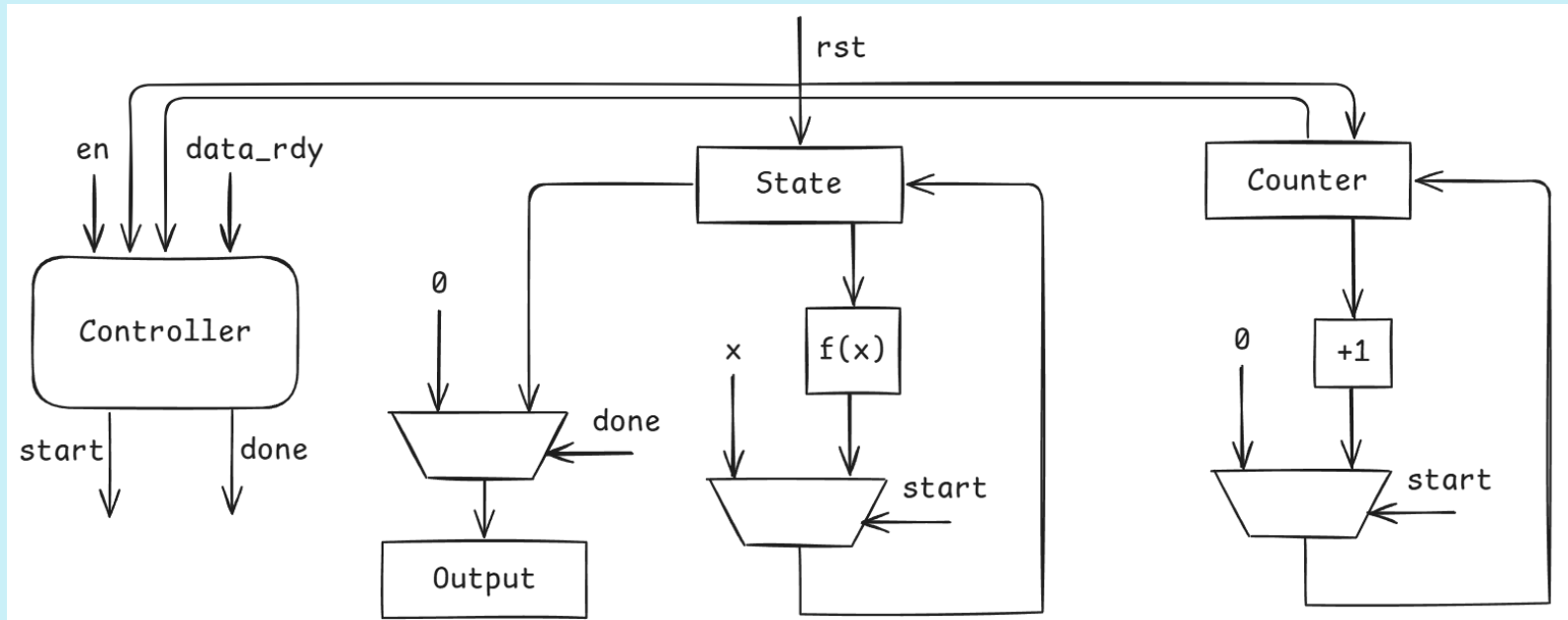

**Thank You!**